# Lab 9-10 Report Nano Processor Design Competition CS 1050 – Computer Organization and Digital Design

Group Members: Chinthana S.K.G. 200093M

Ekanayake E.M.C.L. 200157 Paramulla P.D.N.T. 200444R Rupasinghe R.A.M.T. 200546G

Wickramarathna H.K.G.V.L. 200710F

### **Lab Task**

- The main task in this lab is to create a 4-bit Nano-processor that can handle 8 instructions.
- After that write instructions to add/ subtract 4-bit integers.
- Then verify the developed processor using Vivado simulation.
- Finally, test the code on the basys3 board.

# **Assembly Program**

Table 1 – Instruction Set.

| Instruction | Description  | Format (12-bit instruction)   |
|-------------|--|-------------------------------|
| MOVI R, d   | Move immediate value $d$ to register R, i.e., $R \leftarrow d$ R $\in$ [0, 7], $d \in$ [0, 15] | 10RRR000dddd                  |
| ADD Ra, Rb  | Add values in registers Ra and Rb and store the result in Ra, i.e., Ra ← Ra + Rb               | 0 0 Ra Ra Ra Rb Rb Rb 0 0 0 0 |
|             | $Ra, Rb \in [0, 7]$  |                               |
| NEG R       | 2's complement of registers R, i.e., R $\leftarrow$ – R R $\in$ [0, 7]                         | 01RRR0000000                  |
| JZR R, d    | Jump if value in register R is 0, i.e., If R == 0  | 11RRR0000ddd                  |
|             | PC ← d;  |                               |
|             | Else   |                               |
|             | PC ← PC + 1;   |                               |
|             | $R \in [0, 7], d \in [0, 7]$   |                               |

## Content

- ➤ High-level diagram of the Nano Processor
- Components
  - 3-bit Program Counter (PC)
  - 3-bit Program Counter Adder
  - Program ROM
  - Instruction Decoder
  - Register Bank
  - k-way b-bit Multiplexers
    - o 2-way 3-bit Multiplexer
    - o 2-way 4-bit Multiplexer
    - 8-way 4-bit Multiplexer
  - 4-bit Add/Subtract Unit
  - Slow Clock
  - 7 Segment Display
    - o Look-Up Table
    - o 7 Segment Display
- Nano Processor
- Resource consumption optimizations to the basic program designs, and final LUT/FF counts
- ➤ Additional instructions/features and the Optimization
- Conclusion
- Contribution of team members

# **High-level diagram of the Nano Processor**

 


Figure 1 - High-level diagram of the nanoprocessor.

# 3-bit Program Counter (PC)

# -- Company: -- Engineer: -- Create Date: 07/10/2022 11:20:45 PM -- Design Name: -- Module Name: Add\_3 - Behavioral -- Project Name: -- Target Devices: -- Tool Versions: -- Description: -- Dependencies: -- Revision: -- Revision 0.01 - File Created -- Additional Comments: library IEEE; use IEEE.STD\_LOGIC\_1164.ALL; -- Uncomment the following library declaration if using -- arithmetic functions with Signed or Unsigned values --use IEEE.NUMERIC\_STD.ALL; -- Uncomment the following library declaration if instantiating -- any Xilinx leaf cells in this code. --library UNISIM; --use UNISIM.VComponents.all; entity Add\_3 is Port ( A: in STD\_LOGIC\_VECTOR (2 downto 0); B: in STD\_LOGIC\_VECTOR (2 downto 0); C\_in : in STD\_LOGIC; S: out STD\_LOGIC\_VECTOR (2 downto 0); C\_out : out STD\_LOGIC); end Add\_3;


```
architecture Behavioral of Add_3 is
component FA
  port (
    A: in std_logic;
    B: in std_logic;
    C_in: in std_logic;
    S: out std_logic;
    C_out: out std_logic);
end component;
signal FA0_C,FA1_C,FA2_C: STD_LOGIC;
signal B0,B1,B2: STD_LOGIC_VECTOR (2 downto 0);
begin
FA_0 : FA
  port map (
    A => '1',
    B => B(0),
    C_in => '0',
    S => S(0),
    C_Out => FA0_C);
FA_1: FA
  port map (
    A => '0',
    B => B(1),
    C_in => FA0_C,
    S => S(1),
    C_Out => FA1_C);
FA_2: FA
  port map (
    A = > '0',
    B => B(2),
    C_in => FA1_C,
    S => S(2),
    C_Out => C_Out);
end Behavioral;
Test Bench Code
-- Company:
-- Engineer:
-- Create Date: 07/27/2022 09:51:07 PM
-- Design Name:
-- Module Name: Program_Counter_0_TB - Behavioral
-- Project Name:
```

```
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity Program_Counter_O_TB is
-- Port ();
end Program_Counter_0_TB;
architecture Behavioral of Program_Counter_O_TB is
component Program_Counter
  Port ( Pro Counter Reset : in STD LOGIC;
      Clk: in STD_LOGIC;
      Pro_Counter_Address_In: in STD_LOGIC_VECTOR (2 downto 0);
      Pro_Counter_Address_Out : out STD_LOGIC_VECTOR (2 downto 0) := "000");
end component;
signal reset : std_logic;
signal clk : std_logic := '0';
signal address_in : std_logic_vector(2 downto 0);
signal address_out : std_logic_vector(2 downto 0);
begin
```

```
UUT : Program_Counter
  port map (
    Pro_Counter_Reset => reset,
    Clk => clk,
    Pro_Counter_Address_In => address_in,
    Pro_Counter_Address_Out => address_out
  );
process
begin
  wait for 5ns;
  clk <= NOT clk;
end process;
process
begin
  reset <= '1';
  wait for 50ns;
  reset <= '0';
  address_in <= "000";
  wait for 100ns;
  address_in <= "001";
  wait for 100ns;
  address_in <= "010";
  wait for 100ns;
  address_in <= "011";
  wait for 100ns;
  address_in <= "100";
  wait for 100ns;
  address_in <= "101";
  wait for 100ns;
  address_in <= "110";
  wait for 100ns;
  address_in <= "111";
  wait for 100ns;
```

reset <= '1'; wait;

end process; end Behavioral;

 

## **3-bit Program Counter Adder**


# -- Company: -- Engineer: -- Create Date: 07/10/2022 11:20:45 PM -- Design Name: -- Module Name: Add\_3 - Behavioral -- Project Name: -- Target Devices: -- Tool Versions: -- Description: -- Dependencies: -- Revision: -- Revision 0.01 - File Created -- Additional Comments: library IEEE; use IEEE.STD\_LOGIC\_1164.ALL; -- Uncomment the following library declaration if using -- arithmetic functions with Signed or Unsigned values --use IEEE.NUMERIC\_STD.ALL; -- Uncomment the following library declaration if instantiating -- any Xilinx leaf cells in this code. --library UNISIM; --use UNISIM.VComponents.all; entity Add\_3 is Port ( Add3\_A : in STD\_LOGIC\_VECTOR (2 downto 0); Add3\_B: in STD\_LOGIC\_VECTOR (2 downto 0); Add3\_C\_in: in STD\_LOGIC; Add3\_S: out STD\_LOGIC\_VECTOR (2 downto 0); Add3\_C\_out : out STD\_LOGIC); end Add\_3;

```
architecture Behavioral of Add_3 is
component FA
  port (
     A: in std_logic;
     B: in std_logic;
     C_in: in std_logic;
     S: out std_logic;
     C_out: out std_logic);
end component;
signal FA0_C,FA1_C,FA2_C: STD_LOGIC;
signal B0,B1,B2: STD_LOGIC_VECTOR (2 downto 0);
begin
FA_0 : FA
  port map (
    A \Rightarrow Add3_A(0),
    B => Add3_B(0),
    C_in => '0',
    S \Rightarrow Add3_S(0),
    C_Out => FA0_C);
FA_1: FA
  port map (
     A \Rightarrow Add3_A(1),
     B \Rightarrow Add3_B(1),
     C_in => FA0_C,
     S \Rightarrow Add3_S(1),
     C_Out => FA1_C);
FA_2: FA
  port map (
     A => Add3_A(2),
     B \Rightarrow Add3_B(2),
     C_in => FA1_C,
     S \Rightarrow Add3_S(2),
     C_Out => Add3_C_Out);
end Behavioral;
Test Bench Code
-- Company:
-- Engineer:
-- Create Date: 07/10/2022 11:44:04 PM
-- Design Name:
-- Module Name: TB_Add_3 - Behavioral
-- Project Name:
```

```
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity TB_Add_3 is
-- Port ();
end TB_Add_3;
architecture Behavioral of TB_Add_3 is
component Add_3
  Port ( Add3_A : in STD_LOGIC_VECTOR (2 downto 0);
      Add3_B: in STD_LOGIC_VECTOR (2 downto 0);
      Add3_C_in: in STD_LOGIC;
      Add3_S: out STD_LOGIC_VECTOR (2 downto 0);
      Add3_C_out : out STD_LOGIC);
end component;
signal B1: STD_LOGIC_VECTOR (2 downto 0);
signal S1: STD_LOGIC_VECTOR (2 downto 0);
signal C_out :STD_LOGIC;
begin
  UUT: Add_3
    PORT MAP(
      Add3_A => "001",
      Add3_B => B1,
```

```
Add3_C_in => '0',
Add3_S => S1,
Add3_C_out => C_out);
process
begin
B1 <= "110";
wait for 200ns;
B1 <= "010";
wait for 200ns;
B1 <= "111";
wait;
end process;
```

end Behavioral;

 

# **Program ROM**

```
VHDL Code
-- Company:
-- Engineer:
-- Create Date: 07/10/2022 01:26:48 PM
-- Design Name:
-- Module Name: ROM - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity ROM is
  Port ( Mem_Select : in STD_LOGIC_VECTOR (2 downto 0);
      instruction: out STD_LOGIC_VECTOR (11 downto 0));
end ROM;
architecture Behavioral of ROM is
type rom_type is array(0 to 5) of STD_LOGIC_VECTOR(11 downto 0);
```


```
signal Program_ROM: rom_type := (
    "100010001010", --MOVI R1, 10; R1? 10
    "100100000001", --MOVI R2, 1; R2?1
    "010100000000", --NEG R2; R2?-R2
    "000010100000", --ADD R1, R2; R1? R1 + R2
    "110010000111", --JZR R1, 7; If R1 = 0 jump to line 7
    "110000000011" -- JZR RO, 3; If RO = 0 jump to line 3
    ---need seven
);
begin
instruction <= Program_ROM(to_integer(unsigned(Mem_Select)));</pre>
end Behavioral;
Test Bench Code
-- Company:
-- Engineer:
-- Create Date: 07/27/2022 09:05:33 PM
-- Design Name:
-- Module Name: TB_ROM - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity TB_ROM is
-- Port ();
end TB_ROM;
architecture Behavioral of TB_ROM is
component ROM
  Port ( Mem_Select : in STD_LOGIC_VECTOR (2 downto 0);
   instruction: out STD_LOGIC_VECTOR (11 downto 0));
end component;
signal Mem_Select: STD_LOGIC_VECTOR (2 downto 0);
signal instruction: STD_LOGIC_VECTOR (11 downto 0);
begin
UUT: ROM
  PORT MAP(
  Mem_Select => Mem_Select,
  instruction => instruction);
process
begin
  Mem_Select <= "000";
  wait for 125ns;
  Mem_Select <= "001";
  wait for 125ns;
  Mem_Select <= "010";
  wait for 125ns;
  Mem_Select <= "011";
  wait for 125ns;
  Mem_Select <= "100";
  wait for 125ns;
  Mem_Select <= "101";
  wait for 125ns;
```

```
Mem_Select <= "110";
wait for 125ns;

Mem_Select <= "111";
wait;

end process;
end Behavioral;</pre>
```

 

## **Instruction Decoder**

# **VHDL Code** -- Company: -- Engineer: -- Create Date: 08/01/2022 11:41:48 PM -- Design Name: -- Module Name: inst\_decoder\_unit - Behavioral -- Project Name: -- Target Devices: -- Tool Versions: -- Description: -- Dependencies: -- Revision: -- Revision 0.01 - File Created -- Additional Comments: library IEEE; use IEEE.STD\_LOGIC\_1164.ALL; -- Uncomment the following library declaration if using -- arithmetic functions with Signed or Unsigned values --use IEEE.NUMERIC\_STD.ALL; -- Uncomment the following library declaration if instantiating -- any Xilinx leaf cells in this code. --library UNISIM; --use UNISIM.VComponents.all; entity inst\_Decoder\_unit is Port (inst\_bus: in STD\_LOGIC\_VECTOR (11 downto 0); check\_jump : in STD\_LOGIC\_VECTOR (3 downto 0); register\_en: out STD\_LOGIC\_VECTOR (2 downto 0); register\_sel\_A : out STD\_LOGIC\_VECTOR (2 downto 0); register\_sel\_B: out STD\_LOGIC\_VECTOR (2 downto 0); immediate\_value : out STD\_LOGIC\_VECTOR (3 downto 0); load\_sel : out STD\_LOGIC; jump\_flag: out STD\_LOGIC;

```
add_sub_sel : out STD_LOGIC;
      Addr_jump: out STD_LOGIC_VECTOR (2 downto 0)
      );
end inst_Decoder_unit;
architecture Behavioral of inst_Decoder_unit is
signal pc: STD_LOGIC;
begin
  register_en <= inst_bus(9 downto 7);</pre>
  register_sel_A <= inst_bus(9 downto 7);</pre>
  register_sel_B <= inst_bus(6 downto 4);</pre>
  immediate_value <= inst_bus(3 downto 0);</pre>
  Addr_jump <= inst_bus(2 downto 0);
  process(check_jump)
  begin
  if(check_jump = "0000") then
    pc <= '1';
  else
    pc <= '0';
  end if;
  end process;
  load_sel<=(NOT(inst_bus(11))) OR ((inst_bus(11)) AND (inst_bus(10)));</pre>
  jump_flag <= pc AND (inst_bus(11)) AND (inst_bus(10));</pre>
  add_sub_sel <= (NOT(inst_bus(11))) AND (inst_bus(10));
end Behavioral;
```


#### **Test Bench Code**

-----

```
-- Company:
-- Engineer:
--
-- Create Date: 08/02/2022 12:39:10 AM
-- Design Name:
-- Module Name: inst_decoder_unit_TB - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
```

```
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity inst_decoder_unit_TB is
-- Port ();
end inst_decoder_unit_TB;
architecture Behavioral of inst_decoder_unit_TB is
component inst decoder unit
  Port (inst_bus: in STD_LOGIC_VECTOR (11 downto 0);
     check_jump : in STD_LOGIC_VECTOR (3 downto 0);
     register en: out STD LOGIC VECTOR (2 downto 0);
     register_sel_A : out STD_LOGIC_VECTOR (2 downto 0);
     register_sel_B: out STD_LOGIC_VECTOR (2 downto 0);
     immediate_value : out STD_LOGIC_VECTOR (3 downto 0);
     load sel: out STD LOGIC;
     jump_flag: out STD_LOGIC;
     add_sub_sel : out STD_LOGIC;
     Addr_jump : out STD_LOGIC_VECTOR (2 downto 0)
     );
end component;
signal inst_bus: STD_LOGIC_VECTOR (11 downto 0);
signal register_en,register_sel_A,register_sel_B,Addr_jump :STD_LOGIC_VECTOR (2 downto 0);
signal immediate_value,check_jump : STD_LOGIC_VECTOR (3 downto 0);
signal load_sel,jump_flag,add_sub_sel : STD_LOGIC;
begin
```

```
UUT:inst_decoder_unit
  PORT MAP(
     inst_bus => inst_bus,
     check_jump => check_jump,
     register_en => register_en,
     register_sel_A => register_sel_A,
     register_sel_B => register_sel_B,
     immediate_value => immediate_value,
     load_sel => load_sel,
     jump_flag => jump_flag,
     add_sub_sel => add_sub_sel,
     Addr_jump => Addr_jump
     );
process
begin
  inst_bus <= "100110000101";
  wait for 200ns;
  inst_bus <= "000110010000";
  wait for 200ns;
  inst_bus <= "011010000000";
   wait for 200ns;
   inst_bus <= "111110000010";
   wait;
end process;
end Behavioral;
```

 

# **Register Bank**

# **VHDL Code** -- Company: -- Engineer: -- Create Date: 07/10/2022 03:24:01 PM -- Design Name: -- Module Name: Reg\_Bank - Behavioral -- Project Name: -- Target Devices: -- Tool Versions: -- Description: -- Dependencies: -- Revision: -- Revision 0.01 - File Created -- Additional Comments: library IEEE; use IEEE.STD\_LOGIC\_1164.ALL; -- Uncomment the following library declaration if using -- arithmetic functions with Signed or Unsigned values --use IEEE.NUMERIC\_STD.ALL; -- Uncomment the following library declaration if instantiating -- any Xilinx leaf cells in this code. --library UNISIM; --use UNISIM.VComponents.all; entity Reg\_Bank is Port ( D: in STD\_LOGIC\_VECTOR (3 downto 0); CLK: in STD\_LOGIC; I: in STD\_LOGIC\_VECTOR (2 downto 0); CLR: in STD\_LOGIC; R0 : out STD\_LOGIC\_VECTOR (3 downto 0); R1: out STD\_LOGIC\_VECTOR (3 downto 0);

```
R2 : out STD_LOGIC_VECTOR (3 downto 0);
    R3 : out STD_LOGIC_VECTOR (3 downto 0);
    R4: out STD_LOGIC_VECTOR (3 downto 0);
    R5 : out STD_LOGIC_VECTOR (3 downto 0);
    R6: out STD_LOGIC_VECTOR (3 downto 0);
    R7: out STD_LOGIC_VECTOR (3 downto 0)
  );
end Reg_Bank;
architecture Behavioral of Reg_Bank is
component Decoder_3_to_8
  Port ( I: in STD_LOGIC_VECTOR (2 downto 0);
      EN: in STD LOGIC;
      Y: out STD_LOGIC_VECTOR (7 downto 0));
end component;
component Reg
  Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
     En : in STD_LOGIC;
     Reset: in STD LOGIC;
     Clk: in STD_LOGIC;
     Q: out STD_LOGIC_VECTOR (3 downto 0));
end component;
signal Reg_enable: STD_LOGIC_VECTOR(7 downto 0);
begin
Decoder_3_to_8_0: Decoder_3_to_8
  PORT MAP(
    I => I,
    EN => '1',
    Y => Reg enable);
--Hardcoding RO
Reg_0: Reg
  PORT MAP(
    D => "0000",
    En => Reg_enable(0),
    Reset => CLR,
    CLK => CLK,
    Q \Rightarrow R0;
Reg_1: Reg
  PORT MAP(
```

```
D \Rightarrow D,
    En => Reg_enable(1),
    Reset => CLR,
    CLK => CLK,
    Q \Rightarrow R1);
Reg_2: Reg
  PORT MAP(
    D => D,
    En => Reg_enable(2),
    Reset => CLR,
    CLK => CLK,
    Q \Rightarrow R2;
Reg_3: Reg
  PORT MAP(
    D => D,
    En => Reg_enable(3),
    Reset => CLR,
    CLK => CLK,
    Q => R3);
Reg_4: Reg
   PORT MAP(
    D => D,
    En => Reg_enable(4),
    Reset => CLR,
    CLK => CLK,
    Q => R4);
Reg_5: Reg
   PORT MAP(
    D => D,
    En => Reg_enable(5),
    Reset => CLR,
    CLK => CLK,
    Q => R5);
Reg_6: Reg
   PORT MAP(
    D => D,
    En => Reg_enable(6),
    Reset => CLR,
    CLK => CLK,
    Q \Rightarrow R6;
```

```
Reg_7: Reg
   PORT MAP(
    D => D,
    En => Reg_enable(7),
    Reset => CLR,
    CLK => CLK,
    Q => R7);
end Behavioral;
Test Bench Code
-- Company:
-- Engineer:
-- Create Date: 07/12/2022 11:30:53 AM
-- Design Name:
-- Module Name: TB_Reg_Bank - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity TB_Reg_Bank is
```

```
-- Port ();
end TB_Reg_Bank;
architecture Behavioral of TB_Reg_Bank is
component Reg_Bank
  Port (
    D: in STD_LOGIC_VECTOR (3 downto 0);
    CLK: in STD LOGIC;
    I: in STD_LOGIC_VECTOR (2 downto 0);
    CLR: in STD_LOGIC;
    R0: out STD LOGIC VECTOR (3 downto 0);
    R1 : out STD_LOGIC_VECTOR (3 downto 0);
    R2 : out STD_LOGIC_VECTOR (3 downto 0);
    R3: out STD_LOGIC_VECTOR (3 downto 0);
    R4: out STD_LOGIC_VECTOR (3 downto 0);
    R5: out STD_LOGIC_VECTOR (3 downto 0);
    R6 : out STD_LOGIC_VECTOR (3 downto 0);
    R7: out STD_LOGIC_VECTOR (3 downto 0)
  );
end component;
signal D,R0,R1,R2,R3,R4,R5,R6,R7: STD_LOGIC_VECTOR (3 downto 0);
signal CLR : STD_LOGIC := '0';
signal CLK: STD_LOGIC:= '0';
signal I: STD_LOGIC_VECTOR (2 downto 0);
begin
UUT: Reg_Bank
  PORT MAP(
    D \Rightarrow D,
    I => I,
    CLK => CLK,
    CLR => CLR,
    R0 \Rightarrow R0,
    R1 => R1,
    R2 => R2,
    R3 => R3,
    R4 => R4,
    R5 => R5,
    R6 => R6,
    R7 => R7);
process
  begin
```

```
CLK <= not CLK;
    wait for 50ns;
end process;
process
  begin
    --200546G
    --0011 0000 1111 0110 0010
    --000 110 000 111 101 100 010
    CLR <= '1';
    wait for 100ns;
    CLR <= '0';
    D <= "0010";
    I <= "010";
    wait for 100ns;
    CLR <= '0';
    D <= "0110";
    I <= "100";
    wait for 100ns;
    CLR <= '0';
    D <= "1111";
    I <= "101";
    wait for 100ns;
    CLR <= '0';
    D <= "0000";
    I <= "111";
    wait for 100ns;
    CLR <= '0';
    D <= "0011";
    I <= "110";
    wait for 100ns;
    CLR <= '0';
    D <= "0110";
    I <= "001";
    wait for 100ns;
    CLR <= '0';
    D <= "0111";
    I <= "011";
```


```
wait for 100ns;

CLR <= '1';

wait for 100ns;

end process;

end Behavioral;
```

 

# k-way b-bit Multiplexers

#### 2-way 3-bit Multiplexer


```
VHDL Code
-- Company:
-- Engineer:
-- Create Date: 07/11/2022 12:30:10 PM
-- Design Name:
-- Module Name: mux_2_3 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity mux_2_3_x is
  Port ( mux_2_3_A: in STD_LOGIC_VECTOR (2 downto 0);
      mux_2_3_B: in STD_LOGIC_VECTOR (2 downto 0);
      mux_2_3_C0 : in STD_LOGIC;
      mux_2_3_Q: out STD_LOGIC_VECTOR (2 downto 0));
end mux_2_3_x;
```

```
architecture Behavioral of mux_2_3_x is
component mux_2_1_x
  port(A0 : in STD_LOGIC;
    A1: in STD_LOGIC;
    S: in STD_LOGIC;
    Y: out STD_LOGIC);
end component;
begin
  mux_2_1_0: mux_2_1_x
  port map(
  A0 => mux_2_3_A(0),
  A1 => mux_2_3_B(0),
  S => mux_2_3_C0,
  Y = \max_{2_3} Q(0);
  mux_2_1_1: mux_2_1_x
  port map(
  A0 => mux_2_3_A(1),
  A1 => mux_2_3_B(1),
  S => mux_2_3_C0,
  Y => mux_2_3_Q(1));
  mux_2_1_2: mux_2_1_x
  port map(
  A0 => mux_2_3_A(2),
  A1 => mux_2_3_B(2),
  S => mux_2_3_C0,
  Y => mux_2_3_Q(2);
end Behavioral;
Test Bench Code
-- Company:
-- Engineer:
-- Create Date: 07/26/2022 09:52:22 AM
-- Design Name:
-- Module Name: TB_MUX_2_3 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
```

```
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity TB_MUX_2_3 is
-- Port ();
end TB_MUX_2_3;
architecture Behavioral of TB_MUX_2_3 is
component mux 2 3
port(mux_2_3_A: in STD_LOGIC_VECTOR (2 downto 0);
  mux_2_3_B: in STD_LOGIC_VECTOR (2 downto 0);
  mux_2_3_C0 : in STD_LOGIC;
  mux_2_3_Q0 : out STD_LOGIC_VECTOR (2 downto 0));
end component;
signal A,B: STD_LOGIC_VECTOR (2 downto 0);
signal C0 : STD_LOGIC;
signal Q0: STD_LOGIC_VECTOR (2 downto 0);
begin
UUT: mux_2_3
PORT MAP(
mux_2_3_A => A,
mux_2_3_B => B,
mux_2_3_C0 => C0,
```

```
mux_2_3_Q0 => Q0);

 process
  begin
  A <= "000";
  B <= "111";
  C0 <= '0';
  wait for 20ns;
  C0 <= '1';
  wait;
end process;
end Behavioral;</pre>
```




#### 2-way 4-bit Multiplexer

```
-- Company:
-- Engineer:
-- Create Date: 07/11/2022 12:41:19 PM
-- Design Name:
-- Module Name: mux_2_4 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity mux_2_4 is
  Port ( mux_2_4_A : in STD_LOGIC_VECTOR (3 downto 0);
      mux_2_4_B: in STD_LOGIC_VECTOR (3 downto 0);
      mux_2_4_C0: in STD_LOGIC;
      mux_2_4_Q : out STD_LOGIC_VECTOR (3 downto 0));
end mux_2_4;
architecture Behavioral of mux_2_4 is
```

```
component mux_2_1_x
port(A0: in STD_LOGIC;
  A1: in STD_LOGIC;
  S: in STD_LOGIC;
  Y: out STD_LOGIC);
end component;
begin
mux_2_1_0: mux_2_1_x
  port map(
  A0 => mux_2_4_A(0),
  A1 => mux_2_4_B(0),
  S => mux_2_4_C0,
  Y => mux_2_4_Q(0);
mux_2_1_1: mux_2_1_x
  port map(
  A0 => mux_2_4_A(1),
  A1 => mux_2_4_B(1),
  S => mux_2_4_C0,
  Y => mux_2_4_Q(1);
mux_2_1_2: mux_2_1_x
  port map(
  A0 => mux_2_4_A(2),
  A1 => mux_2_4_B(2),
  S => mux_2_4_C0,
  Y => mux_2_4_Q(2);
mux_2_1_3: mux_2_1_x
  port map(
  A0 => mux_2_4_A(3),
  A1 => mux_2_4_B(3),
  S => mux_2_4_C0,
  Y => mux_2_4_Q(3);
end Behavioral;
Test Bench Code
-- Company:
-- Engineer:
```

```
-- Create Date: 07/26/2022 10:03:30 AM
-- Design Name:
-- Module Name: TB_MUX_2_4 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity TB_MUX_2_4 is
-- Port ();
end TB_MUX_2_4;
architecture Behavioral of TB_MUX_2_4 is
component mux_2_4
port(mux_2_4_A: in STD_LOGIC_VECTOR (3 downto 0);
  mux_2_4_B : in STD_LOGIC_VECTOR (3 downto 0);
  mux_2_4_C0: in STD_LOGIC;
  mux_2_4_Q : out STD_LOGIC_VECTOR (3 downto 0));
end component;
signal A,B: STD_LOGIC_VECTOR (3 downto 0);
signal CO: STD_LOGIC;
signal Q: STD_LOGIC_VECTOR (3 downto 0);
```
 
```
begin
UUT: mux_2_4
  port map(
  mux_2_4_A => A,
  mux_2_4_B=> B,
  mux_2_4_C0 =>C0,
  mux_2_4_Q => Q);
process
begin
A <= "0000";
B <= "1111";
C0 <= '0';
wait for 20ns;
C0 <= '1';
wait;
end process;
end Behavioral;
```



#### 8-way 4-bit Multiplexer

```
-- Company:
-- Engineer:
-- Create Date: 07/11/2022 03:45:53 PM
-- Design Name:
-- Module Name: mux_8_4 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity mux_8_4_x is
Port ( mux_8_4_R0 : in STD_LOGIC_VECTOR (3 downto 0);
    mux_8_4_R1: in STD_LOGIC_VECTOR (3 downto 0);
   mux_8_4_R2: in STD_LOGIC_VECTOR (3 downto 0);
   mux_8_4_R3 : in STD_LOGIC_VECTOR (3 downto 0);
   mux_8_4_R4: in STD_LOGIC_VECTOR (3 downto 0);
   mux_8_4_R5 : in STD_LOGIC_VECTOR (3 downto 0);
   mux_8_4_R6 : in STD_LOGIC_VECTOR (3 downto 0);
   mux_8_4_R7: in STD_LOGIC_VECTOR (3 downto 0);
```

```
mux_8_4_S: in STD_LOGIC_VECTOR (2 downto 0);
   --mux 8 4 EN: in STD LOGIC;
   mux_8_4_Q : out STD_LOGIC_VECTOR (3 downto 0));
end mux_8_4_x;
architecture Behavioral of mux_8_4_x is
component Mux_x
  port(D : in STD_LOGIC_VECTOR (7 downto 0);
    S: in STD_LOGIC_VECTOR (2 downto 0);
    EN : in STD_LOGIC;
    Y: out STD_LOGIC);
end component;
begin
  mux_8_4_0:Mux_x
  port map(
  D(0) => mux_8_4_R0(0),
  D(1) => mux_8_4_R1(0),
  D(2) => mux_8_4_R2(0),
  D(3) => mux_8_4_R3(0),
  D(4) => mux_8_4_R4(0),
  D(5) => mux_8_4_R5(0),
  D(6) => mux_8_4_R6(0),
  D(7) => mux_8_4_R7(0),
  S => mux_8_4_S,
  EN => '1',
  Y => mux_8_4_Q(0);
  mux_8_4_1:Mux_x
  port map(
  D(0) => mux 8 4 RO(1),
  D(1) => mux_8_4_R1(1),
  D(2) => mux_8_4_R2(1),
  D(3) => mux_8_4_R3(1),
  D(4) => mux_8_4_R4(1),
  D(5) => mux_8_4_R5(1),
  D(6) => mux_8_4_R6(1),
  D(7) => mux_8_4_R7(1),
  S = \max_{8_4} S,
  EN => '1',
  Y = \max_{8_4} Q(1);
```

```
mux_8_4_2:Mux_x
  port map(
  D(0) => mux_8_4_R0(2),
  D(1) => mux_8_4_R1(2),
  D(2) => mux_8_4_R2(2),
  D(3) => mux_8_4_R3(2),
  D(4) => mux_8_4_R4(2),
  D(5) => mux_8_4_R5(2),
  D(6) => mux_8_4_R6(2),
  D(7) => mux_8_4_R7(2),
  S = \max_{8_4} S,
  EN => '1',
  Y => mux_8_4_Q(2));
  mux_8_4_3:Mux_x
  port map(
  D(0) => mux_8_4_R0(3),
  D(1) => mux_8_4_R1(3),
  D(2) => mux_8_4_R2(3),
  D(3) => mux_8_4_R3(3),
  D(4) => mux_8_4_R4(3),
  D(5) => mux_8_4_R5(3),
  D(6) => mux_8_4_R6(3),
  D(7) => mux_8_4_R7(3),
  S = \max_{8_4} S,
  EN =>'1',
  Y => mux_8_4_Q(3);
end Behavioral;
Test Bench Code
```

```
-- Company:
```

-- Engineer:

-- Create Date: 07/26/2022 08:44:18 AM

-- Design Name:

-- Module Name: TB\_MUX\_8\_4 - Behavioral

-- Project Name:

-- Target Devices:


-- Tool Versions:

-- Description:

```
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity TB_MUX_8_4 is
-- Port ();
end TB_MUX_8_4;
architecture Behavioral of TB_MUX_8_4 is
component mux_8_4
port(mux_8_4_R0 : in STD_LOGIC_VECTOR (3 downto 0);
  mux_8_4_R1 : in STD_LOGIC_VECTOR (3 downto 0);
  mux_8_4_R2: in STD_LOGIC_VECTOR (3 downto 0);
  mux_8_4_R3 : in STD_LOGIC_VECTOR (3 downto 0);
  mux 8 4 R4: in STD LOGIC VECTOR (3 downto 0);
  mux_8_4_R5 : in STD_LOGIC_VECTOR (3 downto 0);
  mux_8_4_R6 : in STD_LOGIC_VECTOR (3 downto 0);
  mux_8_4_R7 : in STD_LOGIC_VECTOR (3 downto 0);
  mux_8_4_S : in STD_LOGIC_VECTOR (2 downto 0);
  mux_8_4_EN: in STD_LOGIC;
  mux_8_4_Q : out STD_LOGIC_VECTOR (3 downto 0));
end component;
signal R0,R1,R2,R3,R4,R5,R6,R7: STD_LOGIC_VECTOR (3 downto 0);
signal S: STD_LOGIC_VECTOR (2 downto 0);
signal EN:STD_LOGIC;
signal Q: STD_LOGIC_VECTOR (3 downto 0);
```

```
begin
UUT: mux_8_4
PORT MAP(
mux_8_4_R0 => R0,
mux_8_4_R1 => R1,
mux_8_4_R2 => R2,
mux_8_4_R3 => R3,
mux_8_4_R4 => R4,
mux_8_4_R5 => R5,
mux_8_4_R6 => R6,
mux_8_4_R7 => R7,
mux_8_4_S => S,
mux_8_4_EN \Rightarrow EN,
mux_8_4_Q => Q);
process
  begin
  EN <= '1';
  R0 <="0000";
  R1 <="0001";
  R2 <="0010";
  R3 <="0011";
  R4 <="0100";
  R5 <="0101";
  R6 <="0110";
  R7 <="0111";
  S <= "000";
  wait for 20ns;
  S <= "001";
  wait for 20ns;
  S <= "010";
  wait for 20ns;
  S <= "011";
  wait for 20ns;
  S <= "100";
  wait for 20ns;
  S <= "101";
  wait for 20ns;
  S <= "110";
  wait for 20ns;
  S <= "111";
  wait;
end process;
end Behavioral;
```

#### **Time Diagram**

 

#### 4-bit Add / Subtract Unit

#### **VHDL Code**

```
-- Company:
-- Engineer:
-- Create Date: 07/22/2022 02:03:25 AM
-- Design Name:
-- Module Name: Add_Sub - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity Add_Sub is
  Port (add_sub_A: in STD_LOGIC_VECTOR (3 downto 0);
      add_sub_B: in STD_LOGIC_VECTOR (3 downto 0);
      add_sub_out : out STD_LOGIC_VECTOR (3 downto 0);
      add_sub_sel: in STD_LOGIC;
      Overflow: out STD_LOGIC;
      Zero: out STD_LOGIC);
end Add_Sub;
```

```
architecture Behavioral of Add Sub is
component mux_2_4_add_sub
 Port( Mux_A : in STD_LOGIC_VECTOR (3 downto 0);
     Mux_B: in STD_LOGIC_VECTOR (3 downto 0);
     NegMux: in STD_LOGIC;
     Mux_out : out STD_LOGIC_VECTOR (3 downto 0));
end component;
component RCA_4_add_sub
 Port ( Ax: in STD LOGIC VECTOR(3 downto 0);
      Bx : in STD_LOGIC_VECTOR(3 downto 0);
      C_in : in STD_LOGIC;
      result : out STD_LOGIC_VECTOR(3 downto 0);
      C_out : out STD_LOGIC;
      C_out_FA3: out STD_LOGIC);
end component;
signal not_add_sub_B, Mux_out, Result: STD_LOGIC_VECTOR (3 downto 0);
signal C_out,Neg,AS,C_out_FA3:std_logic;
begin
mux_2_4_add_sub_0:mux_2_4_add_sub
 PORT MAP(Mux_A => add_sub_B,
      Mux_B => not_add_sub_B,
      NegMux => Neg,
      Mux_out => Mux_out);
RCA_0:RCA_4_add_sub
 PORT MAP(Ax => add_sub_A,
      Bx => Mux_out,
      C in =>AS,
      result => result,
      C_out => C_out,
      C_out_FA3 => C_out_FA3
      );
process(add_sub_sel)
 begin
 if (add_sub_sel='0') then
   AS<='0';
    Neg<='0'; --not sure
  else
```

```
AS<='1';
Neg<='1'; --not sure
end if;
end process;

not_add_sub_B <= NOT(add_sub_B);
add_sub_out <= result;
Zero <= NOT(result(0) OR result(1) OR result(2) OR result(3));
--Overflow <= C_out_FA3 XOR C_out;
Overflow <= C_out;
end Behavioral;
```


#### **Test Bench Code**

```
-- Company:
-- Engineer: P.D.N.T.Paramulla
-- Create Date: 07/22/2022 04:06:11 AM
-- Design Name: 4 bit add sub unit
-- Module Name: Add_Sub_TB - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
```

-- any Xilinx leaf cells in this code.

```
--library UNISIM;
--use UNISIM.VComponents.all;
entity Add_Sub_TB is
-- Port ();
end Add_Sub_TB;
architecture Behavioral of Add_Sub_TB is
component Add_Sub
  Port (add_sub_A: in STD_LOGIC_VECTOR (3 downto 0);
     add_sub_B : in STD_LOGIC_VECTOR (3 downto 0);
     add sub out: out STD LOGIC VECTOR (3 downto 0);
     add_sub_sel : in STD_LOGIC;
     Overflow: out STD LOGIC;
     Zero: out STD_LOGIC);
end component;
 signal add_sub_A, add_sub_B, add_sub_out : STD_LOGIC_VECTOR(3 downto 0);
signal add_sub_sel,Overflow,Zero: STD_LOGIC;
begin
  UUT: add_sub
  Port map(add_sub_A => add_sub_A,
      add_sub_B => add_sub_B,
      add_sub_out =>add_sub_out,
      add_sub_sel => add_sub_sel,
      Overflow => Overflow,
      Zero=>Zero);
Process
begin
  add_sub_sel <= '0';--for sub
  add sub A <= "0110";
  add_sub_B <= "0010";
  wait for 100ns;
  add_sub_sel <= '1'; --for add
  add sub A <= "1111";
  add_sub_B <= "0001";
  wait;
end process;
```

#### **Time Diagram**

 

#### **Slow Clock**

## **VHDL Code** -- Company: -- Engineer: -- Create Date: 06/14/2022 07:57:47 PM -- Design Name: -- Module Name: Slow\_Clk - Behavioral -- Project Name: -- Target Devices: -- Tool Versions: -- Description: -- Dependencies: -- Revision: -- Revision 0.01 - File Created -- Additional Comments: \_\_\_\_\_\_ library IEEE; use IEEE.STD\_LOGIC\_1164.ALL; -- Uncomment the following library declaration if using -- arithmetic functions with Signed or Unsigned values --use IEEE.NUMERIC\_STD.ALL; -- Uncomment the following library declaration if instantiating -- any Xilinx leaf cells in this code. --library UNISIM; --use UNISIM.VComponents.all; entity Slow\_Clk is Port ( Clk\_in : in STD\_LOGIC; Clk\_out : out STD\_LOGIC); end Slow\_Clk;

```
architecture Behavioral of Slow_Clk is
signal count:integer :=1;
signal Clk_status : std_logic :='0';
begin
process (Clk_in) begin
if (rising_edge(Clk_in)) then
count <=count+1;
if(count = 4) then
Clk_status <= not Clk_status;
Clk_out <= Clk_status;
count <=1;
end if;
end if;
end process;
```

#### **Test Bench Code**

\_\_\_\_\_

```
-- Company:
-- Engineer:
-- Create Date: 06/18/2022 11:01:27 PM
-- Design Name:
-- Module Name: Slow_clk_TB - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
```

library IEEE;

```
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity Slow_clk_TB is
-- Port ();
end Slow_clk_TB;
architecture Behavioral of Slow_clk_TB is
component Slow_clk
Port (Clk_in : in STD_LOGIC;
   Clk_out : out STD_LOGIC);
end component;
signal Clk_in : STD_LOGIC :='0';
signal Clk_out: STD_LOGIC;
begin
 UUT: Slow_Clk
 PORT MAP(
    Clk_in =>Clk_in,
    Clk_out =>Clk_out);
process
begin
  wait for 20ns;
  Clk_in <= NOT(Clk_in);
  end process;
end Behavioral;
```

#### **7 Segment Display**

#### VHDL Code (LUT)

```
-- Company:
-- Engineer:
-- Create Date: 06/28/2022 01:27:20 PM
-- Design Name:
-- Module Name: LUT_16_7 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity LUT 16 7 is
  Port (address: in STD_LOGIC_VECTOR (3 downto 0);
      data: out STD_LOGIC_VECTOR (6 downto 0));
end LUT_16_7;
architecture Behavioral of LUT_16_7 is
type rom_type is array (0 to 15) of STD_LOGIC_VECTOR(6 downto 0);
  signal sevenSegment_ROM : rom_type := (
               "1000000", --0
```

```
"1111001", --1
               "0100100", --2
               "0110000", --3
               "0011001", --4
               "0010010", --5
               "0000010", --6
               "1111000", --7
               "0000000", --8
               "0010000", --9
               "0001000", --a
               "0000011", --b
               "1000110", --c
               "0100001", --d
               "0000110", --e
               "0001110" --f
               );
begin
data <= sevenSegment_ROM(to_integer(unsigned(address)));</pre>
end Behavioral;
Test Bench Code
-- Company:
-- Engineer:
-- Create Date: 06/23/2022 06:21:25 PM
-- Design Name:
-- Module Name: LUT_16_7_TB - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity LUT_16_7_TB is
-- Port ();
end LUT_16_7_TB;
architecture Behavioral of LUT_16_7_TB is
component LUT_16_7
PORT(address: in STD_LOGIC_VECTOR (3 downto 0);
   data: out STD_LOGIC_VECTOR (6 downto 0));
end component;
signal address:STD LOGIC VECTOR (3 downto 0);
signal data:STD_LOGIC_VECTOR (6 downto 0);
begin
UUT:LUT_16_7
  PORT MAP(
    address => address,
    data => data
    );
process
  begin
    address <= "1100";
    wait for 50ns;
    address <= "1111";
    wait for 50ns;
    address <= "1110";
    wait for 50ns;
    address <= "0011";
    wait for 50ns;
   end process;
end Behavioral;
```

## **Nano Processor**

## **VHDL Code** -- Company: -- Engineer: -- Create Date: 08/03/2022 09:56:03 PM -- Design Name: -- Module Name: Nano\_processor - Behavioral -- Project Name: -- Target Devices: -- Tool Versions: -- Description: -- Dependencies: -- Revision: -- Revision 0.01 - File Created -- Additional Comments: library IEEE; use IEEE.STD\_LOGIC\_1164.ALL; -- Uncomment the following library declaration if using -- arithmetic functions with Signed or Unsigned values --use IEEE.NUMERIC\_STD.ALL; -- Uncomment the following library declaration if instantiating -- any Xilinx leaf cells in this code. --library UNISIM; --use UNISIM.VComponents.all; entity Nano\_processor is Port ( Clk : in STD\_LOGIC; Reset0: in STD\_LOGIC;

Sev\_seg: out STD\_LOGIC\_VECTOR (3 downto 0);

To\_LED: out STD\_LOGIC\_VECTOR (3 downto 0));

Zero0 : out STD\_LOGIC; Overflow0 : out STD\_LOGIC;

end Nano\_processor;

```
architecture Behavioral of Nano processor is
component Slow_Clk
 Port ( Clk_in : in STD_LOGIC;
     Clk_out : out STD_LOGIC);
end component;
component Program Counter
 Port ( Pro_Counter_Reset : in STD_LOGIC;
     Clk: in STD_LOGIC;
     Pro Counter Address In: in STD LOGIC VECTOR (2 downto 0);
     Pro_Counter_Address_Out : out STD_LOGIC_VECTOR (2 downto 0));
end component;
component ROM
 Port (Mem Select: in STD LOGIC VECTOR (2 downto 0);
     instruction: out STD_LOGIC_VECTOR (11 downto 0));
end component;
component Add 3
 Port ( Add3_A : in STD_LOGIC_VECTOR (2 downto 0);
     Add3_B: in STD_LOGIC_VECTOR (2 downto 0);
     Add3_C_in: in STD_LOGIC;
     Add3_S: out STD_LOGIC_VECTOR (2 downto 0);
     Add3 C out: out STD LOGIC);
end component;
component mux 2 3 x
  Port ( mux_2_3_A : in STD_LOGIC_VECTOR (2 downto 0);
     mux_2_3_B: in STD_LOGIC_VECTOR (2 downto 0);
     mux_2_3_C0: in STD_LOGIC;
     mux 2 3 Q: out STD LOGIC VECTOR (2 downto 0));
end component;
component inst Decoder unit
 Port (inst_bus: in STD_LOGIC_VECTOR (11 downto 0);
     check jump: in STD LOGIC VECTOR (3 downto 0);
     register_en: out STD_LOGIC_VECTOR (2 downto 0);
     register_sel_A : out STD_LOGIC_VECTOR (2 downto 0);
     register_sel_B : out STD_LOGIC_VECTOR (2 downto 0);
     immediate_value : out STD_LOGIC_VECTOR (3 downto 0);
     load sel: out STD LOGIC;
     jump_flag : out STD_LOGIC;
     add_sub_sel: out STD_LOGIC;
```

```
Addr_jump: out STD_LOGIC_VECTOR (2 downto 0)
     );
end component;
component mux 2 4
  Port ( mux_2_4_A : in STD_LOGIC_VECTOR (3 downto 0);
     mux_2_4_B: in STD_LOGIC_VECTOR (3 downto 0);
     mux 2 4 CO: in STD LOGIC;
     mux 2 4 Q: out STD LOGIC VECTOR (3 downto 0));
end component;
component Register Bank
 Port ( Data : in STD_LOGIC_VECTOR (3 downto 0);
     Clk: in STD LOGIC;
     Reset: in STD LOGIC;
     Enable : in STD_LOGIC_VECTOR (2 downto 0);
     R0: out STD LOGIC VECTOR (3 downto 0);
     R1: out STD_LOGIC_VECTOR (3 downto 0);
     R2: out STD_LOGIC_VECTOR (3 downto 0);
     R3: out STD_LOGIC_VECTOR (3 downto 0);
     R4: out STD LOGIC VECTOR (3 downto 0);
     R5: out STD_LOGIC_VECTOR (3 downto 0);
     R6: out STD_LOGIC_VECTOR (3 downto 0);
     R7: out STD_LOGIC_VECTOR (3 downto 0));
end component;
component mux_8_4_x
 Port ( mux_8_4_R0 : in STD_LOGIC_VECTOR (3 downto 0);
   mux 8 4 R1: in STD LOGIC VECTOR (3 downto 0);
   mux_8_4_R2: in STD_LOGIC_VECTOR (3 downto 0);
   mux_8_4_R3: in STD_LOGIC_VECTOR (3 downto 0);
   mux_8_4_R4: in STD_LOGIC_VECTOR (3 downto 0);
   mux 8 4 R5: in STD LOGIC VECTOR (3 downto 0);
   mux_8_4_R6: in STD_LOGIC_VECTOR (3 downto 0);
   mux_8_4_R7 : in STD_LOGIC_VECTOR (3 downto 0);
   mux 8 4 S: in STD LOGIC VECTOR (2 downto 0);
   mux_8_4_Q : out STD_LOGIC_VECTOR (3 downto 0));
end component;
component Add_Sub
 Port (add sub A: in STD LOGIC VECTOR (3 downto 0);
     add_sub_B: in STD_LOGIC_VECTOR (3 downto 0);
     add_sub_out : out STD_LOGIC_VECTOR (3 downto 0);
     add_sub_sel : in STD_LOGIC;
     Overflow: out STD_LOGIC;
```

```
Zero: out STD_LOGIC);
end component;
signal Slow_Clk_out,Add3_C_out,jump_flag,load_sel,add_sub_sel,Overflow,Zero:STD_LOGIC;
signal
mux_8_4_A_out,immediate_value,add_sub_out,mux_2_4_out,mux_8_4_B_out:STD_LOGIC_VECTO
R (3 downto 0);
signal instruction:STD_LOGIC_VECTOR (11 downto 0);
signal
Pro Counter Address Out,Add3 out,register en,register sel A,register sel B,mux 2 3 out,Addr
jump:STD_LOGIC_VECTOR (2 downto 0);
signal data_bus:STD_LOGIC_VECTOR (31 downto 0);
begin
Slow_Clk_0:Slow_Clk
 Port map ( Clk_in => Clk,
       Clk_out => Slow_Clk_out);
Program_Counter_0:Program_Counter
 Port map(Pro_Counter_Reset => Reset0,
      Clk => Slow_Clk_out,
      Pro_Counter_Address_In => mux_2_3_out,
      Pro Counter Address Out => Pro Counter Address Out);
ROM_0:ROM
 Port map(
      Mem_Select => Pro_Counter_Address_Out,
      instruction => instruction);
Add_3_0:Add_3
 Port map(Add3 A \Rightarrow "001",
      Add3_B => Pro_Counter_Address_Out,
      Add3_C_in => '0',
      Add3_S =>Add3_out,
      Add3 C out =>Add3 C out);
mux_2_3_x_0:mux_2_3_x
 Port map(mux_2_3_A =>Add3_out,
      mux_2_3_B =>Addr_jump,
      mux_2_3_C0 =>jump_flag,
      mux_2_3_Q => mux_2_3_out
    );
inst_Decoder_unit_0:inst_Decoder_unit
 Port map(inst bus => instruction,
     check_jump => mux_8_4_A_out,
```

```
register_en => register_en,
     register sel A => register sel A,
     register_sel_B => register_sel_B,
     immediate_value => immediate_value,
     load sel => load sel,
     jump_flag => jump_flag,
     add_sub_sel => add_sub_sel,
     Addr_jump => Addr_jump
     );
mux_2_4_0:mux_2_4
  Port map(mux 2 4 A => immediate value,
      mux_2_4_B => add_sub_out,
      mux_2_4_C0 \Rightarrow load_sel,
      mux_2_4_Q => mux_2_4_out
       );
Register_Bank_0:Register_Bank
  Port map(Data=>mux_2_4_out,
     Clk => Slow_Clk_out,
     Reset => Reset0,
     Enable => register_en,
     R0 => data_bus(3 downto 0),
     R1 => data_bus(7 downto 4),
     R2 => data_bus(11 downto 8),
     R3 => data bus(15 downto 12),
     R4 => data_bus(19 downto 16),
     R5 => data_bus(23 downto 20),
     R6 \Rightarrow data bus(27 downto 24),
     R7 => data_bus(31 downto 28)
     );
mux 8 4 x 0:mux 8 4 x
  Port map(mux_8_4_R0 => data_bus(3 downto 0),
      mux_8_4_R1 \Rightarrow data_bus(7 downto 4),
      mux 8 4 R2 => data bus(11 downto 8),
      mux_8_4_R3 => data_bus(15 downto 12),
      mux 8 4 R4 => data bus(19 downto 16),
      mux_8_4_R5 \Rightarrow data_bus(23 downto 20),
      mux_8_4_R6 => data_bus(27 downto 24),
      mux_8_4_R7 => data_bus(31 downto 28),
      mux_8_4_S => register_sel_A,
      mux_8_4_Q => mux_8_4_A_out
   );
```

```
mux_8_4_x_1:mux_8_4_x
   Port map(mux 8 4 R0 => data bus(3 downto 0),
        mux_8_4_R1 => data_bus(7 downto 4),
        mux_8_4_R2 => data_bus(11 downto 8),
        mux_8_4_R3 => data_bus(15 downto 12),
        mux_8_4_R4 \Rightarrow data_bus(19 downto 16),
        mux_8_4_R5 => data_bus(23 downto 20),
        mux_8_4_R6 => data_bus(27 downto 24),
        mux 8 4 R7 => data bus(31 downto 28),
        mux_8_4_S => register_sel_B,
       mux_8_4_Q => mux_8_4_B_out
       );
Add Sub 0:Add Sub
  Port map(add_sub_A => mux_8_4_A_out,
       add_sub_B => mux_8_4_B_out,
      add_sub_out =>add_sub_out,
      add_sub_sel => add_sub_sel,
      Overflow => Overflow,
      Zero => Zero
      );
Sev_seg <=data_bus(31 downto 28);</pre>
Zero0 <= Zero;
Overflow0 <= Overflow;
To_LED <= data_bus(31 downto 28);
end Behavioral;
Test Bench Code
-- Company:
-- Engineer:
-- Create Date: 08/04/2022 12:40:19 AM
-- Design Name: Control unit
-- Module Name: Control_Unit_TB - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
```

```
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity Control_Unit_TB is
-- Port ();
end Control_Unit_TB;
architecture Behavioral of Control_Unit_TB is
component Control_Unit
  Port ( Clk_in : in STD_LOGIC;
      Reset in: in STD LOGIC;
      Seven_seg_out: out STD_LOGIC_VECTOR (6 downto 0);
      Led_out : out STD_LOGIC_VECTOR (3 downto 0);
      Overflow out: out STD LOGIC;
      Zero_out : out STD_LOGIC);
end component;
signal Clk in: STD LOGIC:='0';
signal Reset_in,Overflow_out,Zero_out : STD_LOGIC;
signal Seven_seg_out : STD_LOGIC_VECTOR (6 downto 0);
signal Led_out : STD_LOGIC_VECTOR (3 downto 0);
begin
UUT: Control_Unit
  Port map(Clk_in => Clk_in,
      Reset in => Reset in,
      Seven_seg_out => Seven_seg_out,
      Led_out => Led_out,
      Overflow_out => Overflow_out,
      Zero_out => Zero_out );
```


```
process
begin
wait for 5ns;
Clk_in <=NOT(Clk_in);
end process;

process
begin
Reset_in <='1';
wait for 140ns;


Reset_in <='0';
wait;
end process;

end Behavioral;
```

#### **Time Diagram**

 

#### **Schematic Diagram**

 

# Resource consumption optimizations to the basic program designs, and final LUT/FF counts

| . Slice Logic         |   |      |   |       |   |           |   |       |
|-----------------------|---|------|---|-------|---|-----------|---|-------|
| Site Type             | + | Used | + | Fixed | + | Available | + | Util% |
| Slice LUTs*           | 1 | 38   | ī | 0     | ı | 20800     | 1 | 0.18  |
| LUT as Logic          | ı | 38   | Ī | 0     | Ī | 20800     | ı | 0.18  |
| LUT as Memory         | I | 0    | Ī | 0     | Ī | 9600      | I | 0.00  |
| Slice Registers       | I | 49   | I | 0     | I | 41600     | I | 0.12  |
| Register as Flip Flop | I | 49   | Ī | 0     | I | 41600     | I | 0.12  |
| Register as Latch     | I | 0    | Ī | 0     | I | 41600     | I | 0.00  |
| F7 Muxes              | I | 0    | Ī | 0     | I | 16300     | I | 0.00  |
| F8 Muxes              | I | 0    | Ī | 0     | I | 8150      | I | 0.00  |
|                       | + |      | + |       | + |           | + | +     |

#### Additional instructions/features and the Optimization

As for optimizations, our main concern was towards the instruction decoder. We identified the repeated use of 'If' loops along with the inefficient extraction of data from the instructions read as potential issues that could be further perfected.

Hence the repeated 'If' loops were replaced by logic gates while the instruction data that was read at the initialization of the instruction decoder was sliced and assigned then and there for later usage.

Even more, we made a slight improvement within the adder-subtractor unit by replacing the Two mux enablers which were responsible for invertion of a signal and adding a logic 1 to the end bit respectively, with a signal enabler which returned the same functionality hence reducing the number of signals that had to be passed back and forth.

Our main concern with the last implementation of the Nano processor was the presence of 11 latches. After the modifications mentioned above, we brought the latches count to 0. Even more, the usage of LUTs dropped from 41 to 38 due to the replacement of multiple repeated 'If' loops.

### **Conclusion**

- The main objective of this lab is to develop a larger component using simple components.
- The development of the instruction decoder, register bank, and program ROM led to the creation of the nano processor.
- Also, we create an 8-way 4-bit multiplexer using an 8-way 1-bit multiplexer. Similarly, we use 2 way 1-bit multiplexer to create the 2-way 3-bit multiplexer and 2-way 4-bit multiplexer.
- We evaluated the accuracy of the internal components by simulating several inputs.
- In addition, the component can be made more efficient by using tri-state buffers to create multiplexers.
- This design can be made more complex and larger by expanding the storage of the register bank and program ROM.
- Finally, we can improve the component by reducing the fundamental logic gates and adding more features.

## **Contribution of team members**

| Task                                    | Group Member                 | Hours Spent |  |  |
|---|------------------------------|-------------|--|--|
| Design Code for ROM                     | Rupasinghe R.A.M.T.          | 2 Hours     |  |  |
| Test Bench for ROM                      | Rupasinghe R.A.M.T.          | 1 Hour      |  |  |
| Design Code for Registers               | Rupasinghe R.A.M.T.          | 2 Hours     |  |  |
| Test Bench for Registers                | Rupasinghe R.A.M.T.          | 1 Hour      |  |  |
| Design Code for all the<br>Multiplexers | Wickramarathna<br>H.K.G.V.L. | 2 Hours     |  |  |
| Test Bench for Multiplexers             | Wickramarathna<br>H.K.G.V.L. | 1 Hour      |  |  |
| Design Code for Instruction Decoder     | Paramulla P.D.N.T.           | 3 Hours     |  |  |
| Test Bench for Instruction Decoder      | Paramulla P.D.N.T.           | 1 Hour      |  |  |
| Design Code for Program<br>Counter      | Ekanayake E.M.C.L.           | 2 Hours     |  |  |
| Test Bench for Program Counter          | Ekanayake E.M.C.L.           | 1 Hour      |  |  |
| Design Code for Add/Sub<br>Unit         | Chinthana S.K.G.             | 3 Hours     |  |  |
| Test Bench for Add/Sub Unit             | Chinthana S.K.G.             | 1 Hour      |  |  |
| Final Processor Design Code             | Everyone                     | 6 Hours     |  |  |
| Test Bench for final<br>Processor       | Everyone                     | 3 Hours     |  |  |
| Final Project report                    | Everyone                     | 1 Hour      |  |  |
| Total Tim                               | 30 Hours                     |             |  |  |